



Project Report – CSE332

Topic: 16-bit Processor



NORTH SOUTH UNIVERSITY

Center of Excellence in Higher Education

The first private university in Bangladesh

Name: Md.Tahrim Faroque Tushar

ID: 1621148642

Name: Abdur Rab Dhruba

ID: 1712441642

Name: Kazi Nabiul Alam

ID: 1711217642

Name: Alisa Hossain

ID: 1522014042

Sec: 10

Date: 18-04-2019

Submitted To:

Prof. Dr. Khaleda Ali (KDA1)

Department of Electrical and Computer Engineering

1. Number of Operands: R-format->3 operands

I-format->2 operands

2. Types Of operand: Register-Register based or, Load-Store Based

3. Operations: Opcode is 4 bits and functionality is 3 bits, so total 7 bits are reserved for different operations. By using those bits, we can do 128 operations. Because in binary, for example if we have 2 bits, we can $2^2 = 4$ operations. We can assign them or, select them by using multiplexers (MUX) such as 00, 01, 10, 11. So, with 7 bits we can do $2^7 = 128$ operations.

4. Operations Type:

Arithmetic Operation:

- 1) Addition
- 2) Subtraction
- 3) Multiplication
- 4) Division
- 5) Immediate Addition

Logical Operation:

- 1) AND
- 2) OR
- 3) NOT

Branch Type Operations:

- 1) Branch on equal
- 2) Branch on not equal
- 3) Branch on greater than
- 4) Branch on greater than or equal
- 5) Branch on less than
- 6) Branch on less than or equal

5 from Arithmetic, 3 from Logical and 6 from branch category

Operation	Type	Format	Opcode	funct	Instruction
ADD	Arithmetic	R-format	1010	000	ADD r_0, r_1, r_2
SUB	Arithmetic	R-format	1010	010	SUB r_0, r_1, r_2
AND	Logical	R-format	1010	100	AND r_3, r_4, r_5
OR	Logical	R-format	1010	101	OR r_3, r_4, r_5
ADDI	Arithmetic	I-format	0011	XXX	ADDI $r_8, r_7, 100$
BEQ	Conditional Branch	I-format	0010	XXX	beq $r_5, r_6, 100$
SLT	Logical	R-format	1010	011	slt r_5, r_6, r_7
LW	Load-store	I-format	0000	XXX	lw $r_5, (r_6)0$
SW	Load-store	I-format	0001	XXX	sw $r_5, (r_6)0$

5. Formats:

R-format:

Name	Bit Fields				
Opcode	r_s (1 st source)	r_t (2 nd source)	r_d (destination)	funct	
4 bits	3 bits	3 bits	3 bits	3 bits	

I-format:

Name	Bit Fields		
Opcode	r_s (1 st source)	r_t (destination)	Immediate/address
4 bits	3 bits	3 bits	6 bits

6. List of Registers:

Registers	Values
r_0	000
r_1	001
r_2	010
r_3	011
r_4	100
r_5	101
r_6	110
r_7	111

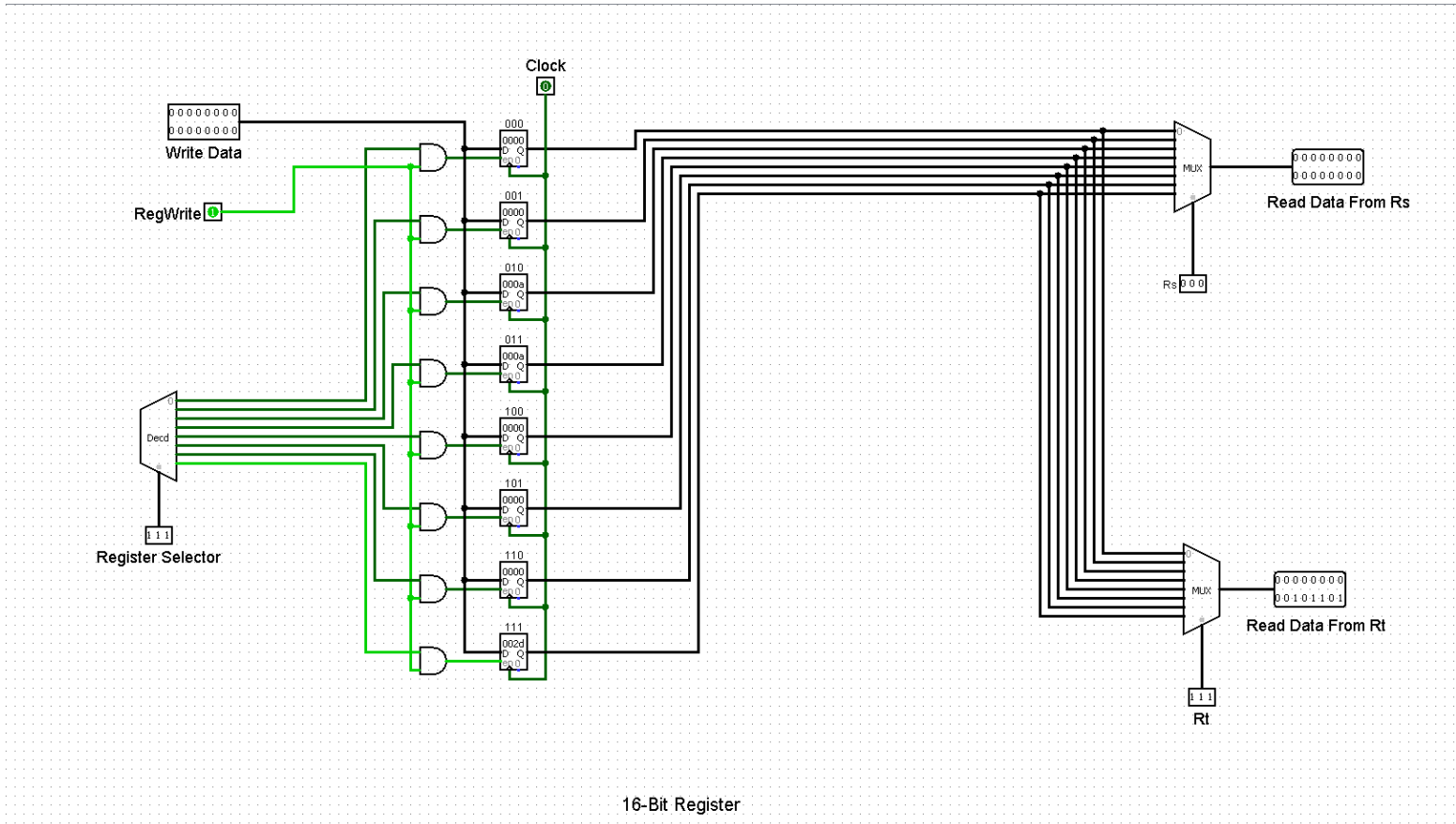


Fig: 16-bit Register

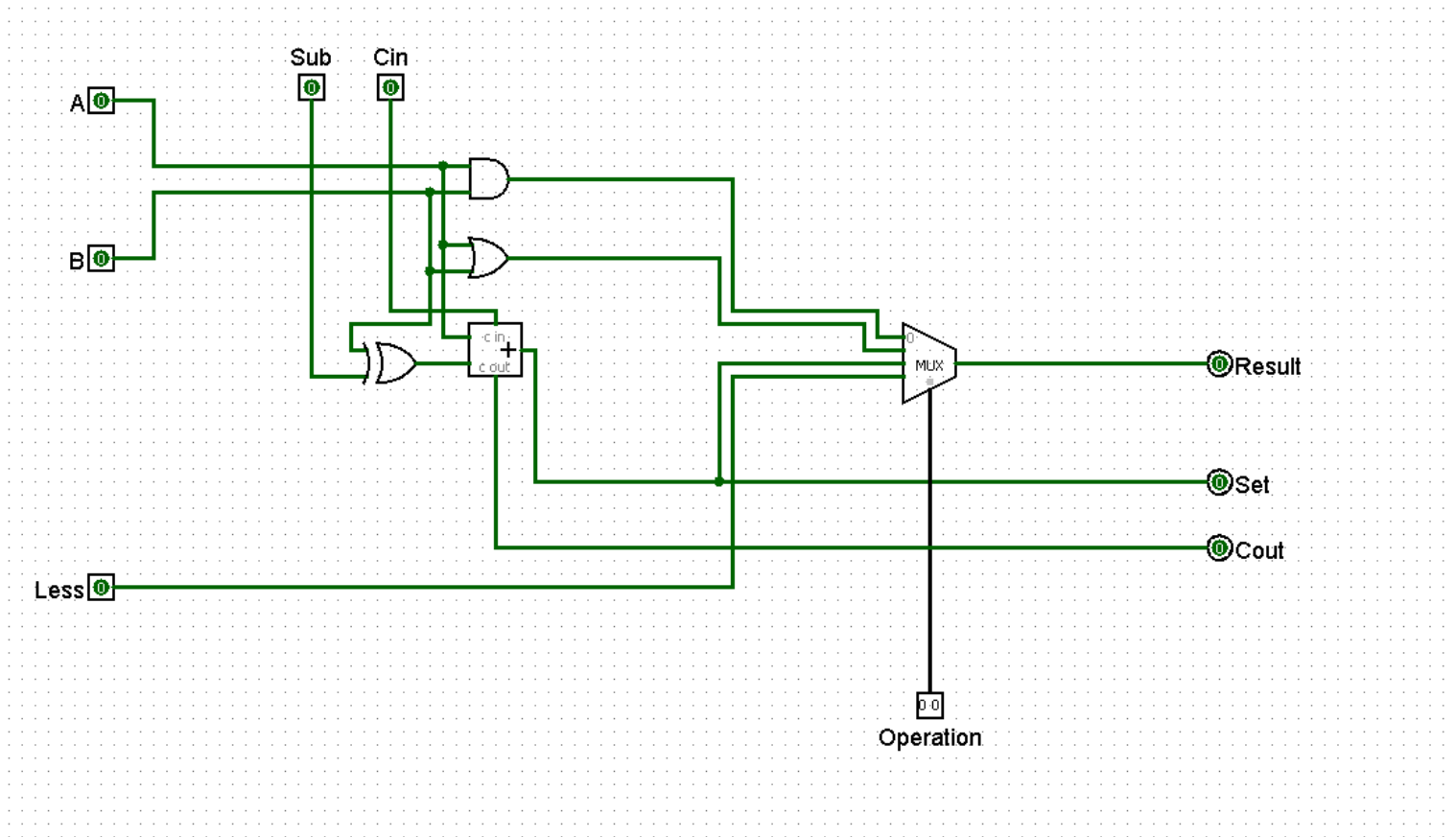


Fig: 1-bit ALU

 


Fig: 16-bit ALU

*Control Unit:

Im	Op Code	R e g D st	ALU Src	Memto Reg	Reg Write	Mem Read	Mem Wr	PC Src	ALU Op1	ALU Op2
R	1010	1	0	0	1	0	0	0	1	0
LW	0000	0	1	1	1	1	0	0	0	0
SW	0001	0	1	0	0	0	1	0	0	0
BEQ	0010	0	0	0	0	0	0	1	0	1
ADDI	0011	0	1	0	1	0	0	0	0	0

 


Fig: Control unit

* ALU Control Unit:

ALUOp1	ALUOp1	F2	F1	F0	Bin	S1	S0	
1	0	1	0	0	0	0	0	AND
1	0	1	0	1	0	0	1	OR
1	0	0	0	0	0	1	0	ADD
1	0	0	1	0	1	1	0	SUB
0	0	x	x	x	0	1	0	ADD
1	0	0	1	1	1	1	1	SLT
0	1	x	x	x	1	1	0	SUB

 


Fig: ALU Control unit

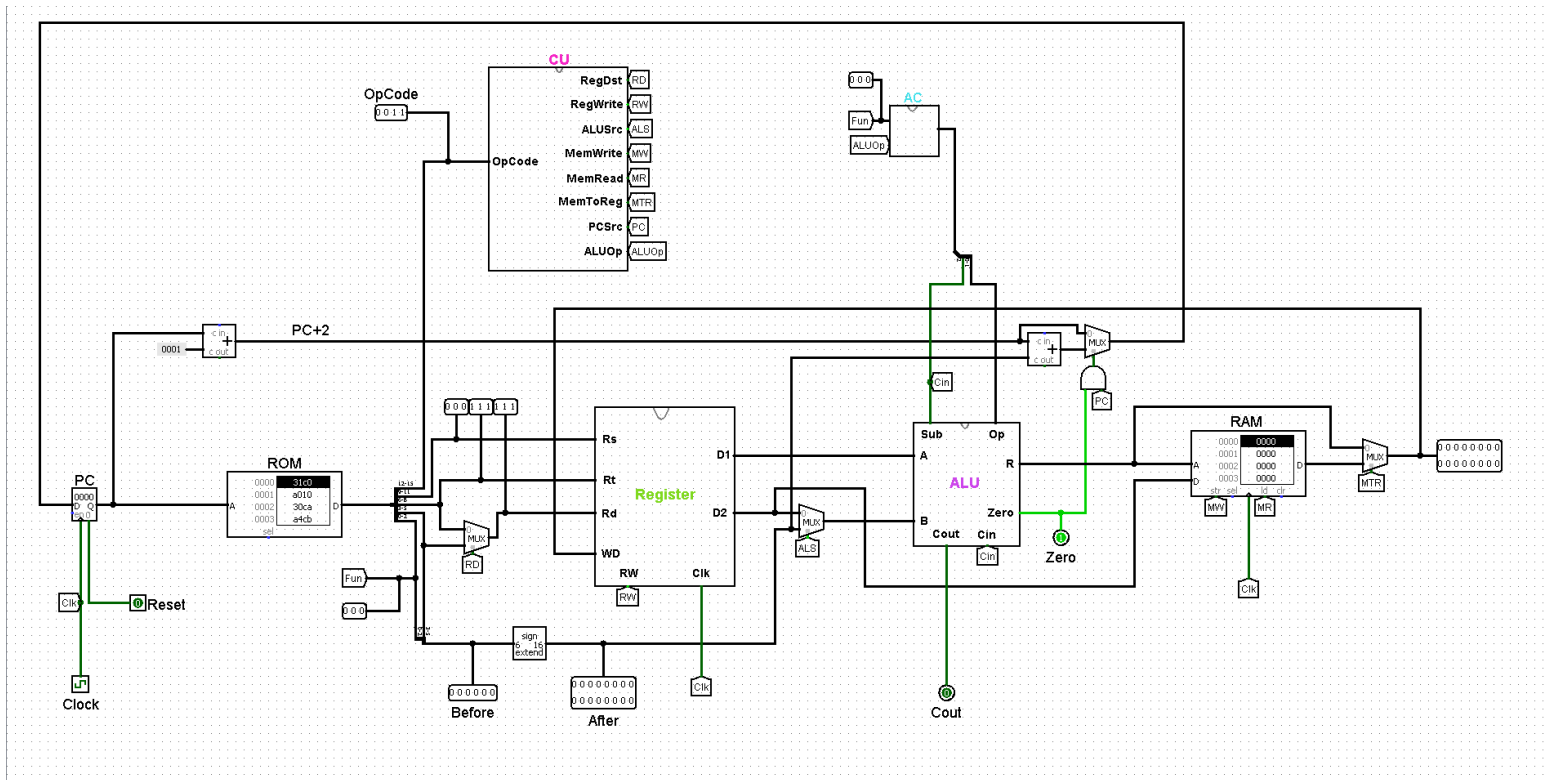


Fig: 16-bit Processor/Datapath

```
compiler_core.py × assembly_code.txt × machine_code.txt ×
1  ADDI r7, r0, 0
2  ADD r2, r0, r0
3  ADDI r3, r0, 10
4  SLT r1, r2, r3
5  BEQ r1, r0, 5
6  LW r4, 0 (r5)
7  ADD r7, r7, r4
8  ADDI r2, r2, 1
9  ADDI r5, r5, 1
10 BEQ r0, r0, -7
11 SW r7, 11 (r0)
```

Fig: Assembly Code

```
compiler_core.py × hex_code.txt × assembly_code.txt × machine_code.txt ×
1 0011000111000000
2 1010000000010000
3 0011000011001010
4 1010011010001011
5 0010000001000101
6 0000101100000000
7 1010100111111000
8 0011010010000001
9 0011101101000001
10 0010000000001001
11 0001111000001011
12
```

Fig: Binary Machine Code


```
1 v2.0 raw
2 31c0 a010 30ca a4cb 2045 b00 a9f8 3481
3 3b41 2039 1e3b
4
```

Fig: Hexadecimal Output

THANK YOU!